

# Power System Assignment 2

## Set 3

### Group Members:

*Keshav Kishore : 2018EEB1158*

*Mahima Kumawat : 2018EEB1162*

*Preetesh Verma : 2018EEB1171*

### **Common Assumptions:**

- (1) Loads are of constant PQ type.
- (2) Y-Y connection of transformers.
- (3) Y(grounded) in source and load.
- (4) Transformers' impedances are assumed to be on the High tension side.

Theoretical Solutions for the three problems are attached below::

Q1)

From the theoretical calculation, we got complex power,  $S = 60 + 45j$  MVA.

So, we have considered parallel RL load with R consuming active power of 60MW and L consuming reactive power of 45 MVAR.

apsara  
Date: \_\_\_\_\_

①

Sec 1.                      Sec 2.                      Sec 3.

Common base power for system =  $S^b = 100 \text{ MVA}$ .

For section 1:

Base Voltage,  $V_1^b = 11 \text{ kV}$ .

$X_{G1} = 0 \text{ pu}$

For section 2:

Base Voltage,  $V_2^b = 132 \text{ kV}$ .

$$X_{T1, \text{new}}^{\text{pu}} = (0.1) \times \left( \frac{100 \text{ M}}{100 \text{ M}} \right) \times \left( \frac{132 \text{ k}}{132 \text{ k}} \right)^2 = 0.1 \text{ pu}$$

$$X_{T2, \text{new}}^{\text{pu}} = (0.08) \times \left( \frac{100 \text{ M}}{100 \text{ M}} \right) \times \left( \frac{132 \text{ k}}{132 \text{ k}} \right)^2 = 0.08 \text{ pu}$$

Transmission line,  $X_{\text{line}}^{\text{actual}} = 0.5 (\Omega/\text{km}) \times 100 \text{ km} = 50 \Omega$ .

$$Z_{\text{base}} = \frac{(132 \text{ k})^2}{(100 \text{ M})}$$

$$Z_{\text{line}}^{\text{pu}} = \frac{50 \times (100 \text{ M})}{(132 \text{ k})^2} = 0.287 \text{ pu}$$

Section 3: Base voltage,  $V_3^b = 66 \text{ kV}$

Given active power of load,  $P = 60 \text{ MW}$ .  
with  $\text{pf} = 0.8 \text{ lag}$

We know, Active power = (Complex power)  $\times \text{pf}$

$$P = S \times 0.8$$

$$\Rightarrow |\bar{S}| = \frac{60 \text{ M}}{0.8} = 75 \text{ MVA}$$

$$\bar{S} = |\bar{S}| \angle \cos^{-1}(0.8) = 75 \angle 36.87^\circ \text{ MVA}$$

$$= 60 + 45j \text{ MVA}$$

$$\bar{S}^* = 75 \angle -36.87^\circ \text{ MVA}$$

$$\bar{Z}_{\text{act}} = \frac{|V_{\text{line}}|^2}{\bar{S}^*} = \frac{(66 \text{ k})^2}{75 \angle -36.87^\circ (\text{M})}$$

$$\bar{Z}_{\text{act}} = 38.4 + 28.8j = 48 \angle 36.87^\circ$$

$$Z_{\text{base}} = \frac{(66 \text{ k})^2}{(100 \text{ M})}$$

$$\bar{Z}_{\text{pu}} = \frac{(48 \angle 36.87^\circ) \times (100 \text{ M})}{(66 \text{ k})^2} = 0.8815 + 0.661j$$

$$\bar{Z}_{\text{pu}} = 1.1019 \angle 36.87^\circ$$



$$\frac{\bar{I}_{act}}{\bar{I}_b} = \frac{\left( \frac{\bar{V}_{act}}{\bar{Z}_{act}} \right)}{\left( \frac{\bar{V}_b}{\bar{Z}_b} \right)} = \frac{\left( \frac{60k}{48 \angle 36.87} \right)}{\left( \frac{66k \times 100M}{(66k)^2} \right)}$$

$$= \frac{60 \times 66}{100 \times 48 \angle 36.87}$$


$$\bar{I}_{pu} = 0.825 \angle -36.87$$

$$V_1^{pu} - V_2^{pu} = (0.825 \angle -36.87) (0.1j + 0.287j + 0.08j)$$

$$V_1^{pu} - \left( \frac{60k}{66k} \right) = 0.385275 \angle 53.17$$

$$V_1^{pu} = 1.181 \angle 15.136$$
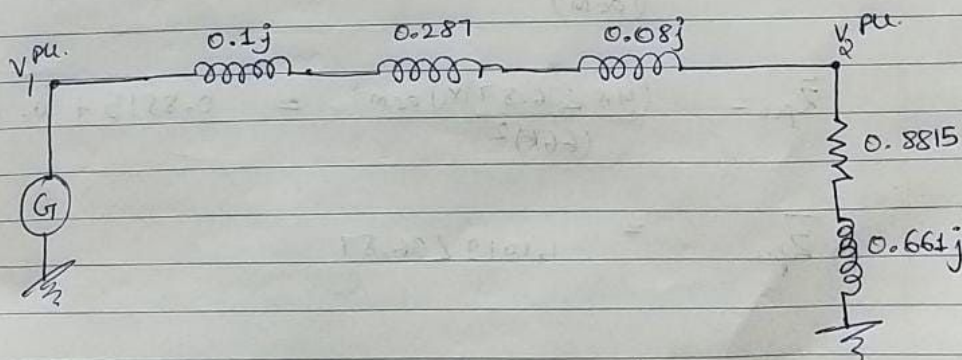
$$V_1^{actual} = 12.991 \angle 15.136 \text{ kV}$$



Line impedance diagram with pu values.

Q2)

apsara  
Date: \_\_\_\_\_

8

②

Base power for system,  $S_b = 5000 \text{ VA}$ .

For Section 1:

Base voltage,  $V_1^b = 250 \text{ V}$ .

For  $G_1$ :

$$Z_{\text{new}}^{\text{pu}} = Z_{\text{old}}^{\text{pu}} \times \left( \frac{\text{KV}_{\text{new}}^b}{\text{KV}_{\text{old}}^b} \right) \times \left( \frac{\text{KV}_{\text{old}}^b}{\text{KV}_{\text{new}}^b} \right)^2$$

$$Z_{G_1}^{\text{pu}} = (0.2j) \left( \frac{5000}{1000} \right) \times \left( \frac{250}{250} \right)^2 = 1j$$

For  $G_2$ :

$$Z_{G_2}^{\text{pu}} = (0.3j) \left( \frac{5000}{2000} \right) \times \left( \frac{250}{250} \right)^2 = 0.75j$$

For Section 2:

$$\frac{V_1^b}{V_2^b} = \frac{250}{800}$$

$$\Rightarrow V_2^b = \left( \frac{800}{250} \times 250 \right) = 800 \text{ V}$$

Page No: \_\_\_\_\_

$\Rightarrow$  Base voltage of sec 2,  $V_2^b = 800V$ .

For  $T_1$ ;

$$Z_{T_1}^{pu} = (0.2j) \times \left( \frac{5000}{4000} \right) \times \left( \frac{800}{800} \right)^2 = 0.25j$$

For  $T_2$ ;

$$Z_{T_2}^{pu} = (0.06j) \left( \frac{5000}{8000} \right) \times \left( \frac{1000}{800} \right)^2 = 0.0586j$$

For T-Line;

$$Z_{TL}^{pu} = \frac{Z^{act}}{Z^b} = \frac{(40 + 150j) \times (5000)}{(800)^2}$$

$$Z_{TL}^{pu} = 0.3125 + 1.172j = 1.213 \angle 75.07$$

Section 3:


$$\frac{V_2^b}{V_3^b} = \frac{1000}{500}$$

$$\Rightarrow V_3^b = \frac{800}{2} = 400V = \text{Base voltage for sec 3.}$$

$$Z_{load}^{pu} = \frac{Z^{act}}{Z^{base}} = \frac{(400)^2}{2500} = 2 \text{ pu}$$

$$\frac{(400)^2}{5000}$$



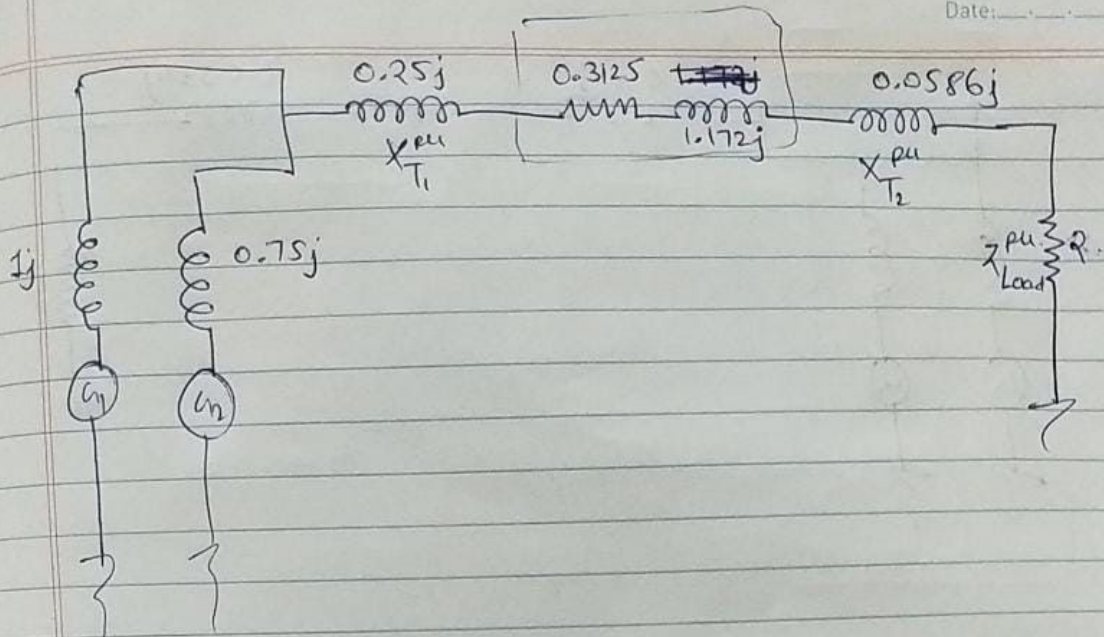


### Q.3

Assumptions:

- Source generator configuration : Y connected
- transformer nominal power =100kVA
- Transmission line Length = 1km
- Load: constant PQ
- Nominal phase to phase voltage at load =1000V
- Load: Y(grounded)


Case 1: Without Tapping

Result of 1:1 transformer

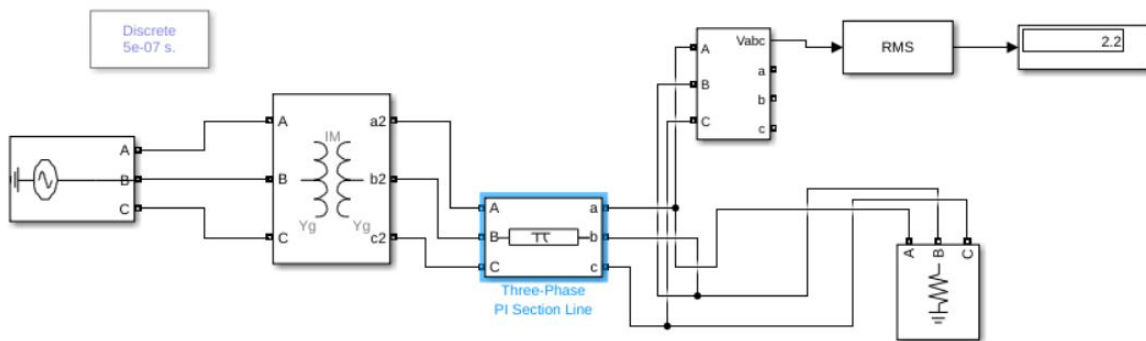

Case 2: With Tapping

Result of 1:0.95

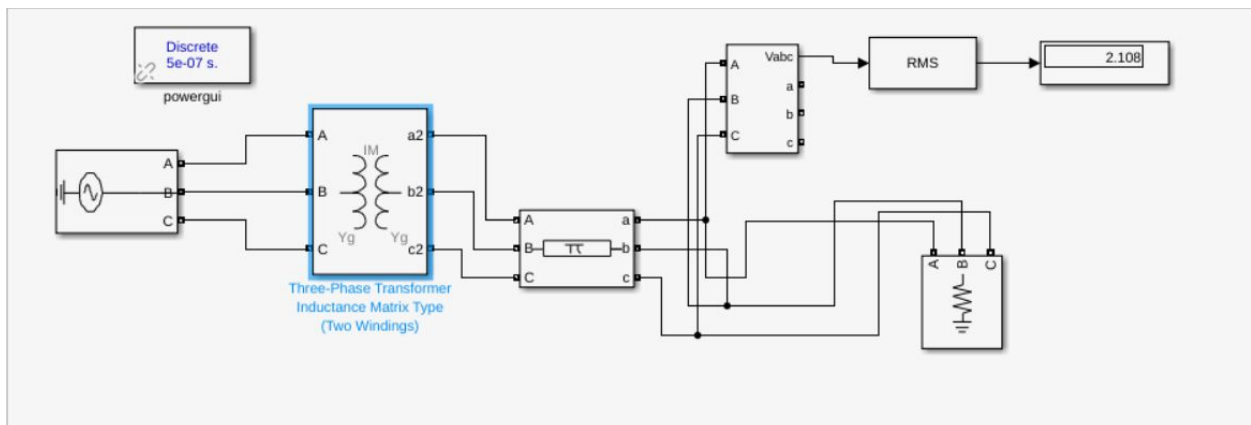

Inference : As turns is decreased at secondary side of tap transformer, output voltage decreases



## Conclusion:

Thus in the end we would like to say that the per unit analysis plays an important role in the analysis of Power Systems and comes handy as dealing with the absolute values could become really cumbersome and also different sections of the System deal with different values of Voltage. So, the Per unit analysis is very important.

For the voltage regulations, we use a tap transformer which allows us to vary the turn ratio to obtain required voltage levels on the secondary side.